

(a)

According to ohms law relation between V , I and R is $V = RI$ Resistance R is $1 \text{ k}\Omega$ Voltage V is 5 V

$$V = RI$$

$$5 \text{ V} = (1000 \Omega)I$$

$$I = \frac{5 \text{ V}}{1000 \Omega}$$

$$I = 5 \text{ mA}$$

Current I is 5 mA

Step 2 of 4

(b)

Voltage V is 5 V Current I is 1 mA

$$V = RI$$

$$5 \text{ V} = R(1 \times 10^{-3} \text{ A})$$

$$R = \frac{5 \text{ V}}{10^{-3} \text{ A}}$$

$$R = 5 \text{ k}\Omega$$

Resistance R is $5 \text{ k}\Omega$

Step 3 of 4

(c)

Resistance R is $10 \text{ k}\Omega$ Current I is 0.1 mA

$$V = RI$$

$$V = (10 \times 10^3 \Omega)(0.1 \times 10^{-3} \text{ A})$$

$$V = 1 \text{ V}$$

Voltage V is 1 V

Step 4 of 4

(d)

Resistance R is 100Ω Voltage V is 5 V

$$V = RI$$

$$5 \text{ V} = (100 \Omega)I$$

$$I = \frac{5 \text{ V}}{100 \Omega}$$

$$I = 50 \text{ mA}$$

Current I is 50 mA

Calculate the source resistance.

$$R_s = \frac{v_{oc}}{i_{sc}}$$

Here,

v_{oc} , is the open circuit voltage.

i_{sc} , is the short circuit voltage.

Substitute **10 mV** for v_{oc} and **10 μ A** for i_{sc} .

$$\begin{aligned} R_s &= \frac{10 \times 10^{-3}}{10 \times 10^{-6}} \\ &= \frac{1}{1 \times 10^{-3}} \\ &= 1 \times 10^3 \\ &= 1 \text{ k}\Omega \end{aligned}$$

Therefore, the source resistance, R_s is **1 k Ω** .

(a)

Value of resistance R is $1\text{ k}\Omega$ Current flowing through $1\text{ k}\Omega$ resistor is 20 mA Power (P) dissipated in the resistor is I^2R

$$\begin{aligned}
 P &= I^2R \\
 &= (20 \times 10^{-3})^2 (1000\ \Omega) \\
 &= 0.4\text{ W}
 \end{aligned}$$

Power (P) dissipated in $1\text{ k}\Omega$ resistor is 0.4 W

For safe operation standard component having power rating greater than 0.4 W should be selected and hence $1/2\text{ W}$ or 1 W or 2 W power rating components are used.

Step 2 of 7

(b)

Value of resistance R is $1\text{ k}\Omega$ Current flowing through $1\text{ k}\Omega$ resistor is 40 mA Power (P) dissipated in the resistor is I^2R

$$\begin{aligned}
 P &= I^2R \\
 &= (40 \times 10^{-3})^2 (1000\ \Omega) \\
 &= 1.6\text{ W}
 \end{aligned}$$

Power (P) dissipated in $1\text{ k}\Omega$ resistor is 1.6 W

For safe operation standard component having power rating greater than 1.6 W should be selected and hence 2 W power rating components are used

Step 3 of 7

(c)

Value of resistance R is $100\text{ k}\Omega$ Current flowing through $100\text{ k}\Omega$ resistor is 1 mA Power (P) dissipated in the resistor is I^2R

$$\begin{aligned}
 P &= I^2R \\
 &= (1 \times 10^{-3})^2 (100000\ \Omega) \\
 &= 0.1\text{ W}
 \end{aligned}$$

Power (P) dissipated in $100\text{ k}\Omega$ resistor is 0.1 W

For safe operation standard component having power rating greater than 0.1 W should be selected and hence $1/8\text{ W}$ or $1/4\text{ W}$ or $1/2\text{ W}$ or 1 W or 2 W power rating components are used

Step 4 of 7

(d)

Value of resistance R is $10\text{ k}\Omega$ Current flowing through $10\text{ k}\Omega$ resistor is 4 mA Power (P) dissipated in the resistor is I^2R

$$\begin{aligned}
 P &= I^2R \\
 &= (4 \times 10^{-3})^2 (10000\ \Omega) \\
 &= 0.16\text{ W}
 \end{aligned}$$

Power (P) dissipated in $10\text{ k}\Omega$ resistor is 0.16 W

For safe operation standard component having power rating greater than 0.16 W should be selected and hence $1/4\text{ W}$ or $1/2\text{ W}$ or 1 W or 2 W power rating components are used

Step 5 of 7

(e)

Value of resistance R is $1\text{ k}\Omega$ Voltage drop across the resistance is 20 V Power (P) dissipated in the resistor is $\frac{V^2}{R}$

$$\begin{aligned}
 P &= \frac{V^2}{R} \\
 &= \frac{(20)^2}{1\text{ k}\Omega} \\
 &= 0.4\text{ W}
 \end{aligned}$$

Power (P) dissipated in $1\text{ k}\Omega$ resistor is 0.4 W

For safe operation standard component having power rating greater than 0.4 W should be selected and hence $1/2\text{ W}$ or 1 W or 2 W power rating components are used

Step 6 of 7

(f)

Value of resistance R is $1\text{ k}\Omega$ Voltage drop across the resistance is 11 V Power (P) dissipated in the resistor is $\frac{V^2}{R}$

$$\begin{aligned}
 P &= \frac{V^2}{R} \\
 &= \frac{(11)^2}{1\text{ k}\Omega} \\
 &= 0.121\text{ W}
 \end{aligned}$$

Step 7 of 7

Power (P) dissipated in $1\text{ k}\Omega$ resistor is 0.121 W

For safe operation standard component having power rating greater than 0.121 W should be selected and hence $1/8\text{ W}$ or $1/4\text{ W}$ or $1/2\text{ W}$ or 1 W or 2 W power rating components are used

Draw the circuit diagram.

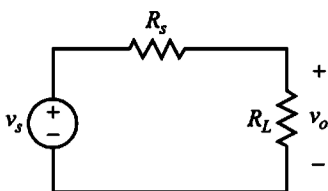


Figure 1

Step 2 of 6

The output voltage that appears across the load resistance is,

$$v_o = v_s \left(\frac{R_L}{R_L + R_s} \right)$$

Calculate the output voltage for $R_L = 100 \text{ k}\Omega$.

$$\begin{aligned} v_o &= v_s \left(\frac{R_L}{R_L + R_s} \right) \\ &= (10 \times 10^{-3}) \left(\frac{100 \times 10^3}{100 \times 10^3 + 1 \times 10^3} \right) \\ &= (10 \times 10^{-3}) \left(\frac{100}{101} \right) \\ &= 9.9 \text{ mV} \end{aligned}$$

Therefore, the output voltage, v_o for $R_L = 100 \text{ k}\Omega$ is **9.9 mV**.

Step 3 of 6

Calculate the output voltage for $R_L = 10 \text{ k}\Omega$.

$$v_o = v_s \left(\frac{R_L}{R_L + R_s} \right)$$

Substitute 10×10^3 for R_L , 1×10^3 for R_s and 10 mV for v_s .

$$\begin{aligned} v_o &= v_s \left(\frac{R_L}{R_L + R_s} \right) \\ &= (10 \times 10^{-3}) \left(\frac{10 \times 10^3}{10 \times 10^3 + 1 \times 10^3} \right) \\ &= (10 \times 10^{-3}) \left(\frac{10}{11} \right) \\ &= 9.1 \text{ mV} \end{aligned}$$

Therefore, the output voltage, v_o for $R_L = 10 \text{ k}\Omega$ is **9.1 mV**.

Step 4 of 6

Calculate the output voltage for $R_L = 1 \text{ k}\Omega$.

$$v_o = v_s \left(\frac{R_L}{R_L + R_s} \right)$$

Substitute 1×10^3 for R_L , 1×10^3 for R_s and 10 mV for v_s .

$$\begin{aligned} v_o &= v_s \left(\frac{R_L}{R_L + R_s} \right) \\ &= (10 \times 10^{-3}) \left(\frac{1 \times 10^3}{1 \times 10^3 + 1 \times 10^3} \right) \\ &= (10 \times 10^{-3}) \left(\frac{1}{2} \right) \\ &= 5 \text{ mV} \end{aligned}$$

Therefore, the output voltage, v_o for $R_L = 1 \text{ k}\Omega$ is **5 mV**.

Step 5 of 6

Calculate the output voltage for $R_L = 100 \Omega$.

$$v_o = v_s \left(\frac{R_L}{R_L + R_s} \right)$$

Substitute 100 for R_L , 1×10^3 for R_s and 10 mV for v_s .

$$\begin{aligned} v_o &= v_s \left(\frac{R_L}{R_L + R_s} \right) \\ &= (10 \times 10^{-3}) \left(\frac{100}{100 + 1 \times 10^3} \right) \\ &= (10 \times 10^{-3}) \left(\frac{100}{1100} \right) \\ &= 0.9 \text{ mV} \end{aligned}$$

Therefore, the output voltage, v_o for $R_L = 100 \Omega$ is **0.9 mV**.

Step 6 of 6

The output voltage is 80 % of the source voltage.

That is, $v_o = 0.8 v_s$.

Write the formula for output voltage.

$$v_o = v_s \left(\frac{R_L}{R_L + R_s} \right)$$

Substitute $1 \text{ k}\Omega$ for R_s and $0.8 v_s$ for v_o .

$$0.8 v_s = v_s \left(\frac{R_L}{R_L + 1 \times 10^3} \right)$$

$$0.8 = \left(\frac{R_L}{R_L + 1 \times 10^3} \right)$$

$$0.8 R_L + 800 = R_L$$

$$0.2 R_L = 800$$

$$R_L = 4000 \Omega$$

$$= 4 \text{ k}\Omega$$

Therefore, the load resistance, R_L is **4 kΩ**.

(a)

Resistance R is $1 \text{ k}\Omega$ Current I is 5 mA According to ohms law $V = IR$

$$\begin{aligned} V &= IR \\ &= (5 \times 10^{-3} \text{ A})(1000 \Omega) \\ &= 5 \text{ V} \end{aligned}$$

Voltage V is 5 V According to power law $P = VI$

$$\begin{aligned} P &= VI \\ &= (5 \text{ V})(5 \times 10^{-3} \text{ A}) \\ &= 0.025 \text{ W} \end{aligned}$$

Power P is 0.025 W

Step 2 of 5

(b)

Voltage V is 5 V Current I is 1 mA According to ohms law $V = IR$

$$\begin{aligned} V &= IR \\ 5 \text{ V} &= (1 \times 10^{-3} \text{ A})R \\ R &= \frac{5 \text{ V}}{(1 \times 10^{-3} \text{ A})} \\ R &= 5 \text{ k}\Omega \end{aligned}$$

Resistance R is $5 \text{ k}\Omega$ According to power law $P = VI$

$$\begin{aligned} P &= VI \\ &= (5 \text{ V})(1 \times 10^{-3} \text{ A}) \\ &= 0.005 \text{ W} \end{aligned}$$

Power P is 0.005 W

Step 3 of 5

(c)

Voltage V is 10 V Power P is 100 mW According to power law $P = VI$

$$\begin{aligned} P &= VI \\ (100 \times 10^{-3} \text{ W}) &= (10 \text{ V})I \\ I &= \frac{(100 \times 10^{-3} \text{ W})}{(10 \text{ V})} \\ I &= 10 \text{ mA} \end{aligned}$$

Current I is 10 mA According to ohms law $V = IR$

$$\begin{aligned} V &= IR \\ 10 \text{ V} &= (10 \times 10^{-3} \text{ A})(R) \\ R &= \frac{10 \text{ V}}{(10 \times 10^{-3} \text{ A})} \\ R &= 1 \text{ k}\Omega \end{aligned}$$

Resistance R is $1 \text{ k}\Omega$

Step 4 of 5

(d)

Current I is 1 mA Power P is 1 mW According to power law $P = VI$

$$\begin{aligned} P &= VI \\ (1 \times 10^{-3} \text{ W}) &= V(1 \times 10^{-3} \text{ A}) \\ V &= 1 \text{ V} \end{aligned}$$

Voltage V is 1 V According to ohms law $V = IR$

$$\begin{aligned} V &= IR \\ 1 \text{ V} &= (1 \times 10^{-3} \text{ A})(R) \\ R &= \frac{1 \text{ V}}{(1 \times 10^{-3} \text{ A})} \\ R &= 1 \text{ k}\Omega \end{aligned}$$

Resistance R is $1 \text{ k}\Omega$

Step 5 of 5

(e)

Resistance R is $1 \text{ k}\Omega$ Power P is 1 W Power P is $I^2 R$

$$\begin{aligned} P &= I^2 R \\ 1 \text{ W} &= I^2 (1000 \Omega) \\ I &= \sqrt{\frac{1}{1000}} \text{ A} \\ I &= 0.032 \text{ A} \end{aligned}$$

Current I is 32 mA According to ohms law $V = IR$

$$\begin{aligned} V &= IR \\ &= (32 \times 10^{-3} \text{ A})(1000 \Omega) \\ &= 32 \text{ V} \end{aligned}$$

Voltage V is 32 V

Draw the circuit diagram.

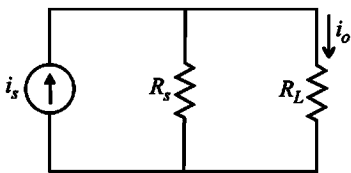


Figure 1

Step 2 of 6

Write the expression for output current using current division rule.

$$i_o = i_s \left(\frac{R_s}{R_s + R_L} \right)$$

Calculate the output voltage for $R_L = 1 \text{ k}\Omega$ by substituting 1×10^3 for R_L , 100×10^3 for R_s and 10×10^{-6} for i_s .

$$\begin{aligned} i_o &= (10 \times 10^{-6}) \left(\frac{100 \times 10^3}{100 \times 10^3 + 1 \times 10^3} \right) \\ &= (10 \times 10^{-6}) \left(\frac{100}{101} \right) \\ &= 9.9 \mu\text{A} \end{aligned}$$

Therefore, the output current, i_o for $R_L = 1 \text{ k}\Omega$ is $\boxed{9.9 \mu\text{A}}$.

Step 3 of 6

Calculate the output voltage for $R_L = 10 \text{ k}\Omega$ by substituting 10×10^3 for R_L , 100×10^3 for R_s and 10×10^{-6} for i_s in the output current expression.

$$\begin{aligned} i_o &= (10 \times 10^{-6}) \left(\frac{100 \times 10^3}{100 \times 10^3 + 10 \times 10^3} \right) \\ &= (10 \times 10^{-6}) \left(\frac{100}{110} \right) \\ &= 9.1 \mu\text{A} \end{aligned}$$

Therefore, the output current, i_o for $R_L = 10 \text{ k}\Omega$ is $\boxed{9.1 \mu\text{A}}$.

Step 4 of 6

Calculate the output voltage for $R_L = 100 \text{ k}\Omega$ by substituting 100×10^3 for R_L , 100×10^3 for R_s and 10×10^{-6} for i_s in the output current expression.

$$\begin{aligned} i_o &= (10 \times 10^{-6}) \left(\frac{100 \times 10^3}{100 \times 10^3 + 100 \times 10^3} \right) \\ &= (10 \times 10^{-6}) \left(\frac{100}{200} \right) \\ &= 5 \mu\text{A} \end{aligned}$$

Therefore, the output current, i_o for $R_L = 100 \text{ k}\Omega$ is $\boxed{5 \mu\text{A}}$.

Step 5 of 6

Calculate the output voltage for $R_L = 1 \text{ M}\Omega$ by substituting 1×10^6 for R_L , 100×10^3 for R_s and 10×10^{-6} for i_s in the output current expression.

$$\begin{aligned} i_o &= (10 \times 10^{-6}) \left(\frac{100 \times 10^3}{100 \times 10^3 + 1 \times 10^6} \right) \\ &= (10 \times 10^{-6}) \left(\frac{100}{1100} \right) \\ &= 0.9 \mu\text{A} \end{aligned}$$

Therefore, the output current, i_o for $R_L = 1 \text{ M}\Omega$ is $\boxed{0.9 \mu\text{A}}$.

Step 6 of 6

The output current is 80 % of the source current.

That is, $i_o = 0.8i_s$.

Write the formula for output current.

$$i_o = i_s \left(\frac{R_s}{R_L + R_s} \right)$$

Substitute $100 \text{ k}\Omega$ for R_s and $0.8i_s$ for i_o .

$$0.8i_s = i_s \left(\frac{100 \times 10^3}{R_L + 100 \times 10^3} \right)$$

$$0.8 = \left(\frac{100 \times 10^3}{R_L + 100 \times 10^3} \right)$$

$$0.8R_L + 80 \times 10^3 = 100 \times 10^3$$

$$0.8R_L = 20 \times 10^3$$

$$R_L = 25 \times 10^3 \Omega$$

$$= 25 \text{ k}\Omega$$

Therefore, the load resistance, R_L is $\boxed{25 \text{ k}\Omega}$.

Determine different resistances with different possible combinations like parallel, series, and series-parallel:

As possible parallel combinations:

Connect all the three resistors in parallel as shown in Figure 1.

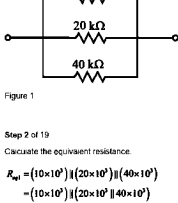


Figure 1

Step 2 of 19

Calculate the equivalent resistance.

$$\begin{aligned} R_{eq1} &= (10 \times 10^3) \parallel (20 \times 10^3) \parallel (40 \times 10^3) \\ &= (10 \times 10^3) \parallel (20 \times 10^3 \parallel 40 \times 10^3) \\ &= 10 \times 10^3 \parallel \left(\frac{(20 \times 10^3)(40 \times 10^3)}{20 \times 10^3 + 40 \times 10^3} \right) \\ &= 10 \times 10^3 \parallel (13.333 \times 10^3) \\ &= \frac{(10 \times 10^3)(13.333 \times 10^3)}{10 \times 10^3 + 13.333 \times 10^3} \\ &= \frac{133.33 \times 10^6}{23.333} \\ &= 5.714 \times 10^3 \Omega \end{aligned}$$

Therefore, the equivalent resistance value is, $R_{eq1} = 5.714 \text{ k}\Omega$.

Step 3 of 19

Connect the two resistors $10 \text{ k}\Omega$ and $20 \text{ k}\Omega$ in parallel as shown in Figure 2.

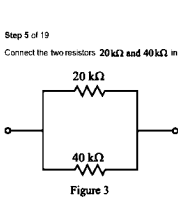


Figure 2

Step 4 of 19

Calculate the equivalent resistance.

$$\begin{aligned} R_{eq2} &= (10 \times 10^3) \parallel (20 \times 10^3) \\ &= \frac{(10 \times 10^3)(20 \times 10^3)}{10 \times 10^3 + 20 \times 10^3} \\ &= \frac{200 \times 10^6}{30} \\ &= 6.67 \times 10^3 \Omega \end{aligned}$$

Therefore, the equivalent resistance value is, $R_{eq2} = 6.67 \text{ k}\Omega$.

Step 5 of 19

Connect the two resistors $20 \text{ k}\Omega$ and $40 \text{ k}\Omega$ in parallel as shown in Figure 3.

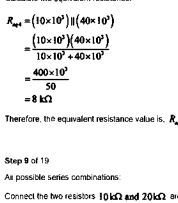


Figure 3

Step 6 of 19

Calculate the equivalent resistance.

$$\begin{aligned} R_{eq3} &= 20 \times 10^3 \parallel 40 \times 10^3 \\ &= \frac{(20 \times 10^3)(40 \times 10^3)}{20 \times 10^3 + 40 \times 10^3} \\ &= \frac{800 \times 10^6}{60} \\ &= 13.333 \times 10^3 \Omega \end{aligned}$$

Therefore, the equivalent resistance value is, $R_{eq3} = 13.333 \text{ k}\Omega$.

Step 7 of 19

Connect the two resistors $10 \text{ k}\Omega$ and $40 \text{ k}\Omega$ in parallel as shown in Figure 4.

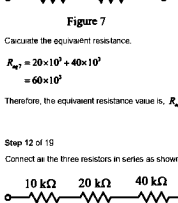


Figure 4

Step 8 of 19

Calculate the equivalent resistance.

$$\begin{aligned} R_{eq4} &= (10 \times 10^3) \parallel (40 \times 10^3) \\ &= \frac{(10 \times 10^3)(40 \times 10^3)}{10 \times 10^3 + 40 \times 10^3} \\ &= \frac{400 \times 10^6}{50} \\ &= 8 \text{ k}\Omega \end{aligned}$$

Therefore, the equivalent resistance value is, $R_{eq4} = 8 \text{ k}\Omega$.

Step 9 of 19

As possible series combinations:

Connect the two resistors $10 \text{ k}\Omega$ and $20 \text{ k}\Omega$ are in series as shown in Figure 5.

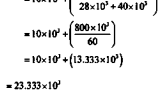


Figure 5

Calculate the equivalent resistance.

$$\begin{aligned} R_{eq5} &= 10 \times 10^3 + 20 \times 10^3 \\ &= 30 \times 10^3 \end{aligned}$$

Therefore, the equivalent resistance value is, $R_{eq5} = 30 \text{ k}\Omega$.

Step 10 of 19

Connect the two resistors $10 \text{ k}\Omega$ and $40 \text{ k}\Omega$ are in series as shown in Figure 6.

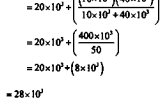


Figure 6

Calculate the equivalent resistance.

$$\begin{aligned} R_{eq6} &= 10 \times 10^3 + 40 \times 10^3 \\ &= 50 \times 10^3 \end{aligned}$$

Therefore, the equivalent resistance value is, $R_{eq6} = 50 \text{ k}\Omega$.

Step 11 of 19

Connect the two resistors $20 \text{ k}\Omega$ and $40 \text{ k}\Omega$ are in series as shown in Figure 7.

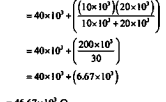


Figure 7

Calculate the equivalent resistance.

$$\begin{aligned} R_{eq7} &= 20 \times 10^3 + 40 \times 10^3 \\ &= 60 \times 10^3 \end{aligned}$$

Therefore, the equivalent resistance value is, $R_{eq7} = 60 \text{ k}\Omega$.

Step 12 of 19

Connect all the three resistors in series as shown in Figure 8.

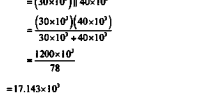


Figure 8

Calculate the equivalent resistance.

$$\begin{aligned} R_{eq8} &= 10 \times 10^3 + 20 \times 10^3 + 40 \times 10^3 \\ &= 70 \times 10^3 \end{aligned}$$

Therefore, the equivalent resistance value is, $R_{eq8} = 70 \text{ k}\Omega$.

Step 13 of 19

All possible series-parallel combinations

Connect the parallel combination of $20 \text{ k}\Omega$ and $40 \text{ k}\Omega$ resistor in series with $10 \text{ k}\Omega$ resistor as shown in Figure 9

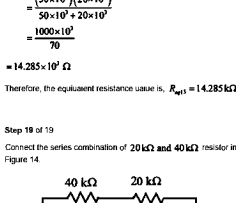


Figure 9

Step 14 of 19

Calculate the equivalent resistance.

$$\begin{aligned} R_{eq9} &= 10 \times 10^3 + (20 \times 10^3 \parallel 40 \times 10^3) \\ &= 10 \times 10^3 + \left(\frac{(20 \times 10^3)(40 \times 10^3)}{20 \times 10^3 + 40 \times 10^3} \right) \\ &= 10 \times 10^3 + \left(\frac{800 \times 10^6}{60} \right) \\ &= 10 \times 10^3 + (13.333 \times 10^3) \\ &= 23.333 \times 10^3 \end{aligned}$$

Therefore, the equivalent resistance value is, $R_{eq9} = 23.333 \text{ k}\Omega$.

Step 15 of 19

Connect the parallel combination of $10 \text{ k}\Omega$ and $40 \text{ k}\Omega$ resistor in series with $20 \text{ k}\Omega$ resistor as shown in Figure 10.

Figure 10

Calculate the equivalent resistance.

$$\begin{aligned} R_{eq10} &= 20 \times 10^3 + (10 \times 10^3 \parallel 40 \times 10^3) \\ &= 20 \times 10^3 + \left(\frac{(10 \times 10^3)(40 \times 10^3)}{10 \times 10^3 + 40 \times 10^3} \right) \\ &= 20 \times 10^3 + \left(\frac{400 \times 10^6}{50} \right) \\ &= 20 \times 10^3 + (8 \times 10^3) \\ &= 28 \times 10^3 \end{aligned}$$

Therefore, the equivalent resistance value is, $R_{eq10} = 28 \text{ k}\Omega$.

Step 16 of 19

Connect the parallel combination of $10 \text{ k}\Omega$ and $20 \text{ k}\Omega$ resistor in series with $40 \text{ k}\Omega$ resistor as shown in Figure 11.

Figure 11

Calculate the equivalent resistance.

$$\begin{aligned} R_{eq11} &= 40 \times 10^3 + (10 \times 10^3 \parallel 20 \times 10^3) \\ &= 40 \times 10^3 + \left(\frac{(10 \times 10^3)(20 \times 10^3)}{10 \times 10^3 + 20 \times 10^3} \right) \\ &= 40 \times 10^3 + \left(\frac{200 \times 10^6}{30} \right) \\ &= 40 \times 10^3 + (6.67 \times 10^3) \\ &= 46.67 \times 10^3 \Omega \\ &= 46.67 \text{ k}\Omega \end{aligned}$$

Therefore, the equivalent resistance value is, $R_{eq11} = 46.67 \text{ k}\Omega$.

Connect the series combination of $10 \text{ k}\Omega$ and $20 \text{ k}\Omega$ resistor in parallel with $40 \text{ k}\Omega$ resistor as shown in Figure 12.

Figure 12

Step 17 of 19

Calculate the equivalent resistance.

$$\begin{aligned} R_{eq12} &= (10 \times 10^3 + 20 \times 10^3) \parallel 40 \times 10^3 \\ &= (30 \times 10^3) \parallel 40 \times 10^3 \\ &= \frac{(30 \times 10^3)(40 \times 10^3)}{30 \times 10^3 + 40 \times 10^3} \\ &= \frac{1200 \times 10^6}{70} \\ &= 17.143 \times 10^3 \end{aligned}$$

Therefore, the equivalent resistance value is, $R_{eq12} = 17.143 \text{ k}\Omega$.

Step 18 of 19

Connect the series combination of $10 \text{ k}\Omega$ and $40 \text{ k}\Omega$ resistor in parallel with $20 \text{ k}\Omega$ resistor as shown in Figure 13.

Figure 13

Calculate the equivalent resistance.

$$\begin{aligned} R_{eq13} &= (10 \times 10^3 + 40 \times 10^3) \parallel 20 \times 10^3 \\ &= (50 \times 10^3) \parallel 20 \times 10^3 \\ &= \frac{(50 \times 10^3)(20 \times 10^3)}{50 \times 10^3 + 20 \times 10^3} \\ &= \frac{1000 \times 10^6}{70} \\ &= 14.285 \times 10^3 \Omega \end{aligned}$$

Therefore, the equivalent resistance value is, $R_{eq13} = 14.285 \text{ k}\Omega$.

Step 19 of 19

Connect the series combination of $20 \text{ k}\Omega$ and $40 \text{ k}\Omega$ resistor in parallel with $10 \text{ k}\Omega$ resistor as shown in Figure 14.

Figure 14

Calculate the equivalent resistance.

$$\begin{aligned} R_{eq14} &= (20 \times 10^3 + 40 \times 10^3) \parallel 10 \times 10^3 \\ &= (60 \times 10^3) \parallel 10 \times 10^3 \\ &= \frac{(60 \times 10^3)(10 \times 10^3)}{60 \times 10^3 + 10 \times 10^3} \\ &= \frac{600 \times 10^6}{70} \\ &= 8.57 \times 10^3 \Omega \end{aligned}$$

Therefore, the equivalent resistance value is, $R_{eq14} = 8.57 \text{ k}\Omega$.

As possible individual resistors are,

$$\begin{aligned} R_{eq15} &= 10 \text{ k}\Omega \\ R_{eq16} &= 20 \text{ k}\Omega \\ R_{eq17} &= 40 \text{ k}\Omega \end{aligned}$$

Therefore, the total possible resistances are $\boxed{17}$.

The values from lowest values to highest values are

$$\begin{aligned} R_{eq1} &= 5.714 \text{ k}\Omega, R_{eq2} = 6.67 \text{ k}\Omega, R_{eq4} = 8 \text{ k}\Omega, R_{eq14} = 8.57 \text{ k}\Omega, R_{eq15} = 10 \text{ k}\Omega, \\ R_{eq9} &= 13.333 \text{ k}\Omega, R_{eq12} = 14.285 \text{ k}\Omega, R_{eq13} = 17.143 \text{ k}\Omega, R_{eq16} = 20 \text{ k}\Omega, \\ R_{eq5} &= 23.333 \text{ k}\Omega, R_{eq10} = 28 \text{ k}\Omega, R_{eq6} = 30 \text{ k}\Omega, R_{eq17} = 40 \text{ k}\Omega, R_{eq11} = 46.67 \text{ k}\Omega \\ R_{eq8} &= 50 \text{ k}\Omega, R_{eq7} = 60 \text{ k}\Omega, R_{eq3} = 70 \text{ k}\Omega \end{aligned}$$

Step 1 of 2

The time period of the sine-wave signal is, $T = 1 \text{ ms}$.

Calculate the frequency.

$$f = \frac{1}{T}$$

Substitute **1 ms** for T .

$$\begin{aligned} f &= \frac{1}{1 \times 10^{-3}} \\ &= 1 \times 10^3 \\ &= \mathbf{1000 \text{ Hz}} \end{aligned}$$

Therefore, the frequency, f is **1000 Hz** .

Step 2 of 2

Calculate the angular frequency.

$$\omega = 2\pi f$$

Substitute **1000 Hz** for f .

$$\begin{aligned} \omega &= 2\pi(1000) \\ &= 2\pi(1000) \\ &= \mathbf{2\pi \times 10^3 \text{ rad/s}} \end{aligned}$$

Therefore, the angular frequency, ω is **$2\pi \times 10^3 \text{ rad/s}$** .

The original resistor value is, $R = 10\text{ k}\Omega$

Calculate the equivalent resistance of two parallel connected resistors.

$$R_{\text{eq}} = R \parallel R_{\text{shunt}}$$

$$= \frac{RR_{\text{shunt}}}{R + R_{\text{shunt}}}$$

The equivalent resistance value is reduced by 1%.

Calculate the shunt resistance value.

$$0.99(10 \times 10^3) = 10 \times 10^3 \parallel R_{\text{shunt}}$$

$$(9.9 \times 10^3) = \frac{(10 \times 10^3)R_{\text{shunt}}}{10 \times 10^3 + R_{\text{shunt}}}$$

$$(9.9 \times 10^3)(10 \times 10^3 + R_{\text{shunt}}) = (10 \times 10^3)R_{\text{shunt}}$$

$$(9.9)(10 \times 10^3 + R_{\text{shunt}}) = 10R_{\text{shunt}}$$

$$99 \times 10^3 + 9.9R_{\text{shunt}} = 10R_{\text{shunt}}$$

$$99 \times 10^3 = 10R_{\text{shunt}} - 9.9R_{\text{shunt}}$$

$$99 \times 10^3 = 0.1R_{\text{shunt}}$$

$$R_{\text{shunt}} = \frac{99 \times 10^3}{0.1}$$

$$R_{\text{shunt}} = 990\text{ k}\Omega$$

Therefore, the value of shunt resistor, R_{shunt} when the combined resistance is reduced by 1%, is

$$\boxed{990\text{ k}\Omega}$$

Step 2 of 8

The equivalent resistance value is reduced by 5%.

Calculate the shunt resistance value.

$$0.95(10 \times 10^3) = 10 \times 10^3 \parallel R_{\text{shunt}}$$

$$(9.5 \times 10^3) = \frac{(10 \times 10^3)R_{\text{shunt}}}{10 \times 10^3 + R_{\text{shunt}}}$$

$$(9.5 \times 10^3)(10 \times 10^3 + R_{\text{shunt}}) = (10 \times 10^3)R_{\text{shunt}}$$

$$(9.5)(10 \times 10^3 + R_{\text{shunt}}) = 10R_{\text{shunt}}$$

$$95 \times 10^3 + 9.5R_{\text{shunt}} = 10R_{\text{shunt}}$$

$$95 \times 10^3 = 10R_{\text{shunt}} - 9.5R_{\text{shunt}}$$

$$95 \times 10^3 = 0.5R_{\text{shunt}}$$

$$R_{\text{shunt}} = \frac{95 \times 10^3}{0.5}\ \Omega$$

$$R_{\text{shunt}} = 190\text{ k}\Omega$$

Therefore, the value of shunt resistor, R_{shunt} when the combined resistance is reduced by 5%, is

$$\boxed{190\text{ k}\Omega}$$

Step 3 of 8

The equivalent resistance value is reduced by 10%.

Calculate the shunt resistance value.

$$0.90(10 \times 10^3) = 10 \times 10^3 \parallel R_{\text{shunt}}$$

$$(9 \times 10^3) = \frac{(10 \times 10^3)R_{\text{shunt}}}{10 \times 10^3 + R_{\text{shunt}}}$$

$$(9 \times 10^3)(10 \times 10^3 + R_{\text{shunt}}) = (10 \times 10^3)R_{\text{shunt}}$$

$$(9)(10 \times 10^3 + R_{\text{shunt}}) = 10R_{\text{shunt}}$$

$$90 \times 10^3 + 9R_{\text{shunt}} = 10R_{\text{shunt}}$$

$$90 \times 10^3 = 10R_{\text{shunt}} - 9R_{\text{shunt}}$$

$$90 \times 10^3 = 1R_{\text{shunt}}$$

$$R_{\text{shunt}} = \frac{90 \times 10^3}{1}\ \Omega$$

$$R_{\text{shunt}} = 90\text{ k}\Omega$$

Therefore, the value of shunt resistor, R_{shunt} when the combined resistance is reduced by 10%, is

$$\boxed{90\text{ k}\Omega}$$

Step 4 of 8

The equivalent resistance value is reduced by 50%.

Calculate the shunt resistance value.

$$0.5(10 \times 10^3) = 10 \times 10^3 \parallel R_{\text{shunt}}$$

$$(5 \times 10^3) = \frac{(10 \times 10^3)R_{\text{shunt}}}{10 \times 10^3 + R_{\text{shunt}}}$$

$$(5 \times 10^3)(10 \times 10^3 + R_{\text{shunt}}) = (10 \times 10^3)R_{\text{shunt}}$$

$$(5)(10 \times 10^3 + R_{\text{shunt}}) = 10R_{\text{shunt}}$$

Step 5 of 8

Simplify further.

$$50 \times 10^3 + 5R_{\text{shunt}} = 10R_{\text{shunt}}$$

$$50 \times 10^3 = 10R_{\text{shunt}} - 5R_{\text{shunt}}$$

$$50 \times 10^3 = 5R_{\text{shunt}}$$

$$R_{\text{shunt}} = \frac{50 \times 10^3}{5}\ \Omega$$

$$R_{\text{shunt}} = 10\text{ k}\Omega$$

Therefore, the value of shunt resistor, R_{shunt} when the combined resistance is reduced by 10%, is

$$\boxed{10\text{ k}\Omega}$$

Step 6 of 8

Calculate the resultant resistance if $R_{\text{shunt}} = 1\text{ M}\Omega$.

$$R_{\text{eq}} = \frac{(10 \times 10^3)(1 \times 10^6)}{(10 \times 10^3) + (1 \times 10^6)}$$

$$= \frac{(10 \times 10^3)(1 \times 10^6)}{1.01 \times 10^6}$$

$$= \frac{10 \times 10^3}{1.01}$$

$$= 9.9\text{ k}\Omega$$

Therefore, the resultant resistance, R_{eq} if $R_{\text{shunt}} = 1\text{ M}\Omega$ is $\boxed{9.9\text{ k}\Omega}$.

Step 7 of 8

Calculate the resultant resistance if $R_{\text{shunt}} = 100\text{ k}\Omega$.

$$R_{\text{eq}} = \frac{(10 \times 10^3)(100 \times 10^3)}{(10 \times 10^3) + (100 \times 10^3)}$$

$$= \frac{(10 \times 10^3)(100 \times 10^3)}{110 \times 10^3}$$

$$= \frac{100 \times 10^3}{11}$$

$$= 9.091\text{ k}\Omega$$

Therefore, the resultant resistance, R_{eq} if $R_{\text{shunt}} = 100\text{ k}\Omega$ is $\boxed{9.091\text{ k}\Omega}$.

Step 8 of 8

If Calculate the resultant resistance if $R_{\text{shunt}} = 10\text{ k}\Omega$.

$$R_{\text{eq}} = \frac{(10 \times 10^3)(10 \times 10^3)}{(10 \times 10^3) + (10 \times 10^3)}$$

$$= \frac{(10 \times 10^3)(10 \times 10^3)}{20 \times 10^3}$$

$$= \frac{100 \times 10^3}{20}$$

$$= 5\text{ k}\Omega$$

Therefore, the resultant resistance, R_{eq} if $R_{\text{shunt}} = 10\text{ k}\Omega$ is $\boxed{5\text{ k}\Omega}$.

Step 1 of 3

(a)

The frequency of the sine wave is, $f = 60 \text{ Hz}$.

The time period is,

$$T = \frac{1}{f}$$

Substitute 60 Hz for f .

$$\begin{aligned} T &= \frac{1}{60} \\ &= 16.7 \times 10^{-3} \text{ s} \\ &= 16.7 \text{ ms} \end{aligned}$$

Therefore, the time period of the sine waveform, T is 16.7 ms .

Step 2 of 3

(b)

The frequency of the sine wave is, $f = 10^{-3} \text{ Hz}$.

The time period is,

$$T = \frac{1}{f}$$

Substitute 10^{-3} Hz for f .

$$\begin{aligned} T &= \frac{1}{10^{-3}} \\ &= 10^3 \\ &= 1000 \text{ s} \end{aligned}$$

Therefore, the time period of the sine waveform, T is 1000 s .

Step 3 of 3

(c)

The frequency of the sine wave is, $f = 1 \text{ MHz}$.

The time period is,

$$T = \frac{1}{f}$$

Substitute 1 MHz for f .

$$\begin{aligned} T &= \frac{1}{1 \times 10^6} \\ &= 1 \times 10^{-6} \text{ s} \\ &= 1 \mu\text{s} \end{aligned}$$

Therefore, the time period of the sine waveform, T is $1 \mu\text{s}$.

Refer to Figure P1.6 in the textbook.

Draw the modified circuit of Figure P1.6.

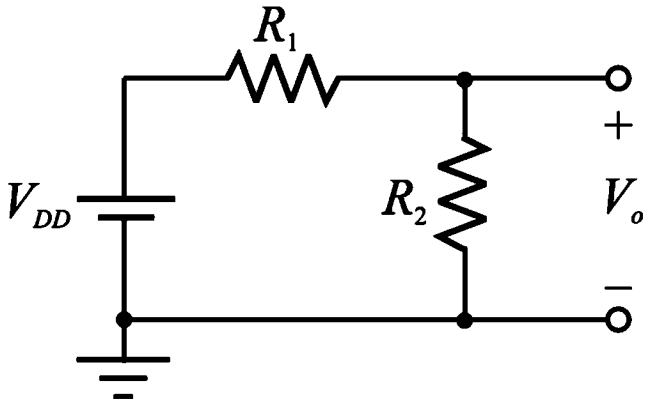


Figure 1

Step 2 of 3

Calculate the output voltage, V_o using voltage division rule.

$$V_o = \left(\frac{R_2}{R_1 + R_2} \right) (V_{DD})$$

Therefore, the output voltage, V_o is $\boxed{\left(\frac{R_2}{R_1 + R_2} \right) (V_{DD})}$.

Draw the circuit diagram, to calculate the Thevenin resistance.

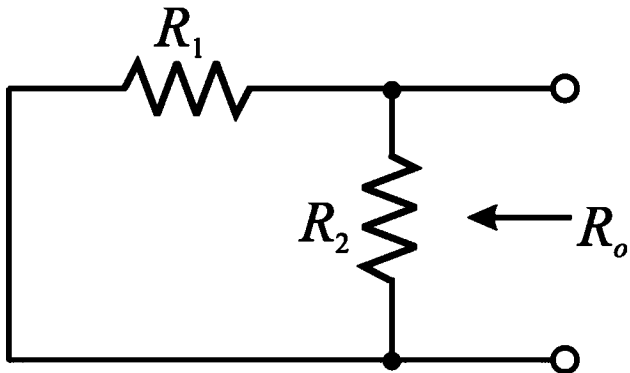


Figure 2

Step 3 of 3

From Figure 2, the equivalent output resistance is,

$$\begin{aligned} R_o &= R_1 \parallel R_2 \\ &= \frac{R_1 R_2}{R_1 + R_2} \end{aligned}$$

Therefore, the output resistance, R_o is $\boxed{\frac{R_1 R_2}{R_1 + R_2}}$.

Ultra High Frequency range is from **470 MHz** to **806 MHz** .

Starting channel is **14**

Channel bandwidth, **BW = 6 MHz** .

Calculate the number of channels.

$$N = \frac{\Delta f}{BW}$$

Substitute 6×10^6 for **BW** .

$$\begin{aligned} N &= \frac{806 \times 10^6 - 470 \times 10^6}{6 \times 10^6} \\ &= \frac{336 \times 10^6}{6 \times 10^6} \\ &= 56 \end{aligned}$$


Therefore, the total number of channels, **N** is **56** .

Calculate the last channel.

$$\begin{aligned} N_{\text{Last}} &= \text{before starting channel} + \text{total number of channels} \\ &= 13 + 56 \\ &= 69 \end{aligned}$$

Therefore, the channels that can be accommodated are **14 to 69** .

Voltage divider circuit shown in the figure 1

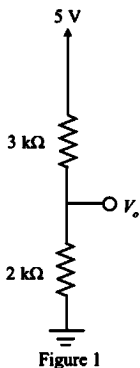**Step 2 of 5**

Power supply voltage V_{DD} is **5 V**

Voltage across **2 kΩ** resistor is,

$$\begin{aligned} V_o &= \frac{V_{DD}}{(3+2) \text{ k}\Omega} (2 \text{ k}\Omega) \\ &= \frac{5 \text{ V}}{(3+2) \text{ k}\Omega} (2 \text{ k}\Omega) \\ &= 2 \text{ V} \end{aligned}$$

Output voltage V_o is **2 V**

Step 3 of 5

Resistors have a manufacturing tolerance of **±5%**

Minimum value of **2 kΩ** resistance is,

$$2 \text{ k}\Omega - \left(\frac{2 \times 5}{100}\right) \text{ k}\Omega = 1.9 \text{ k}\Omega$$

Maximum value of **2 kΩ** resistance is,

$$2 \text{ k}\Omega + \left(\frac{2 \times 5}{100}\right) \text{ k}\Omega = 2.1 \text{ k}\Omega$$

Minimum value of **3 kΩ** resistance is,

$$3 \text{ k}\Omega - \left(\frac{3 \times 5}{100}\right) \text{ k}\Omega = 2.85 \text{ k}\Omega$$

Maximum value of **3 kΩ** resistance is,

$$3 \text{ k}\Omega + \left(\frac{3 \times 5}{100}\right) \text{ k}\Omega = 3.15 \text{ k}\Omega$$

Step 4 of 5

Minimum output voltages of the circuit is obtained when we use the minimum value of resistances **1.9 kΩ** and maximum resistance **3.15 kΩ**

Voltage across **1.9 kΩ** resistor is,

$$\begin{aligned} V_o &= \frac{V_{DD}}{(3.15+1.9) \text{ k}\Omega} (1.9 \text{ k}\Omega) \\ &= \frac{5 \text{ V}}{(3.15+1.9) \text{ k}\Omega} (1.9 \text{ k}\Omega) \\ &= 1.88 \text{ V} \end{aligned}$$

Output voltage V_o is **1.88 V**

Step 5 of 5

Maximum output voltages of the circuit is obtained when we use the maximum value of resistances **2.1 kΩ** and minimum value of resistance **2.85 kΩ**

Voltage across **2.1 kΩ** resistor is,

$$\begin{aligned} V_o &= \frac{V_{DD}}{(2.85+2.1) \text{ k}\Omega} (2.1 \text{ k}\Omega) \\ &= \frac{5 \text{ V}}{(2.85+2.1) \text{ k}\Omega} (2.1 \text{ k}\Omega) \\ &= 2.12 \text{ V} \end{aligned}$$

Output voltage V_o is **2.12 V**

Extreme output voltages of voltage divider circuit is **1.88 V** and **2.12 V**

Refer to Figure 1.5 in the textbook for square wave signal.

The Fourier series for the signal is,

$$v(t) = \frac{4V}{\pi} \left(\sin \omega_b t + \frac{1}{3} \sin 3\omega_b t + \frac{1}{5} \sin 5\omega_b t + \dots \right)$$

Calculate the total power, P .

$$P = \frac{1}{T} \int_0^T \frac{v^2}{R} dt$$

$$= \frac{1}{RT} \int_0^T (V)^2 dt$$

$$= \frac{V^2}{RT} \int_0^T (1) dt$$

$$= \frac{V^2}{RT} [t]_0^T$$

$$= \frac{V^2}{RT} [T - 0]$$

$$= \frac{V^2}{RT} (T)$$

$$P = \frac{V^2}{R} \dots (1)$$

Step 2 of 6

Calculate the total power by summing the contribution of each harmonic component.

$$P = \frac{v^2}{R}$$

$$= P_1 + P_3 + P_5 + \dots$$

$$= \frac{\left(\frac{V_1}{\sqrt{2}}\right)^2}{R} + \frac{\left(\frac{V_3}{\sqrt{2}}\right)^2}{R} + \frac{\left(\frac{V_5}{\sqrt{2}}\right)^2}{R} + \dots$$

$$= \frac{1}{2R} \left[\frac{4V}{\pi} \right]^2 + \frac{1}{2R} \left[\frac{4V}{3\pi} \right]^2 + \frac{1}{2R} \left[\frac{4V}{5\pi} \right]^2 + \dots$$

$$= \frac{16V^2}{2\pi^2 R} \left(1 + \frac{1}{9} + \frac{1}{25} + \dots \right)$$

$$= \frac{V^2}{R} \left[\frac{8}{\pi^2} \left(1 + \frac{1}{9} + \frac{1}{25} + \dots \right) \right]$$

Step 3 of 6

The value of $\frac{8}{\pi^2} \left(1 + \frac{1}{9} + \frac{1}{25} + \dots \right)$ is nearly equal to 1.

Consider the calculation of the infinite series in the parentheses has a sum that approaches $\frac{\pi^2}{8}$.

Therefore, the total power will be as follows:

$$P = \frac{V^2}{R} \left[\frac{8}{\pi^2} \left(\frac{\pi^2}{8} \right) \right]$$

$$P = \frac{V^2}{R} \dots (2)$$

From equations (1) and (2), it is clear that the two approaches are equal.

Step 4 of 6

Calculate the fraction of energy in its fundamental.

$$E_1 = \frac{8}{\pi^2} (1)$$

$$= 0.81$$

Therefore, the fraction of energy in its fundamental, E_1 is **0.81**.

Calculate the fraction of energy in its first five harmonics.

$$E_5 = \frac{8}{\pi^2} \left(1 + \frac{1}{9} + \frac{1}{25} \right)$$

$$= 0.93$$

Therefore, the fraction of energy in its first five harmonics, E_5 is **0.93**.

Step 5 of 6

Calculate the fraction of energy in its first seven harmonics.

$$E_7 = \frac{8}{\pi^2} \left(1 + \frac{1}{9} + \frac{1}{25} + \frac{1}{49} \right)$$

$$= 0.95$$

Therefore, the fraction of energy in its first seven harmonics, E_7 is **0.95**.

Calculate the fraction of energy in its first nine harmonics.

$$E_9 = \frac{8}{\pi^2} \left(1 + \frac{1}{9} + \frac{1}{25} + \frac{1}{49} + \frac{1}{81} \right)$$

$$= 0.96$$

Therefore, the fraction of energy in its first nine harmonics, E_9 is **0.96**.

Step 6 of 6

Calculate the fraction of energy in its first three harmonics.

$$E_3 = \frac{8}{\pi^2} \left(1 + \frac{1}{9} \right)$$

$$= 0.9$$

$$= 90\%$$

Hence, the fraction of energy in its first three harmonics, E_3 is **90%**.

Therefore, **90%** of the energy of the square wave is in the first **3** harmonics.

Each resistor value is $10\text{ k}\Omega$

Battery voltage is 9 V .

(i)

Connect all the resistors in series as shown in Figure 1.

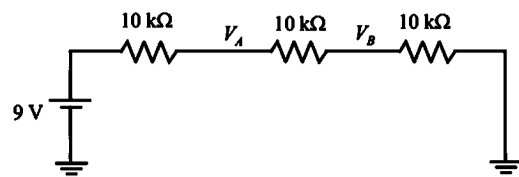


Figure 1

Step 2 of 8

Calculate the voltage, V_A using voltage divider rule.

$$V_A = \left(\frac{10\text{ k}\Omega + 10\text{ k}\Omega}{10\text{ k}\Omega + 10\text{ k}\Omega + 10\text{ k}\Omega} \right) (9\text{ V})$$

$$= 6\text{ V}$$

Calculate the equivalent output resistance.

$$R_o = (10\text{ k}\Omega + 10\text{ k}\Omega) \parallel (10\text{ k}\Omega)$$

$$= 20\text{ k}\Omega \parallel 10\text{ k}\Omega$$

$$= \frac{(20\text{ k}\Omega)(10\text{ k}\Omega)}{20\text{ k}\Omega + 10\text{ k}\Omega}$$

$$= 6.667\text{ k}\Omega$$

Therefore, the output resistance, R_o is $6.667\text{ k}\Omega$.

Step 3 of 8

Calculate the voltage, V_B using voltage divider rule.

$$V_B = \left(\frac{10\text{ k}\Omega}{10\text{ k}\Omega + 10\text{ k}\Omega + 10\text{ k}\Omega} \right) (9\text{ V})$$

$$= \left(\frac{1}{3} \right) (9)$$

$$= 3\text{ V}$$

Calculate the equivalent output resistance.

$$R_o = (10\text{ k}\Omega) \parallel (10\text{ k}\Omega + 10\text{ k}\Omega)$$

$$= 20\text{ k}\Omega \parallel 10\text{ k}\Omega$$

$$= \frac{(20\text{ k}\Omega)(10\text{ k}\Omega)}{20\text{ k}\Omega + 10\text{ k}\Omega}$$

$$= 6.667\text{ k}\Omega$$

Therefore, the output resistance, R_o is $6.667\text{ k}\Omega$.

Step 4 of 8

(ii)

Draw the circuit diagram with series parallel resistors.

These are two cases,

Case (a):

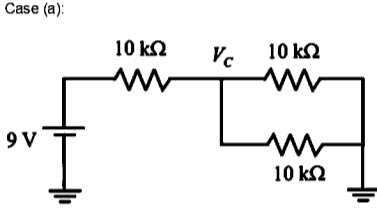


Figure 2

Step 5 of 8

Calculate the voltage, V_C using voltage divider rule.

$$V_C = \left(\frac{10\text{ k}\Omega \parallel 10\text{ k}\Omega}{10\text{ k}\Omega + (10\text{ k}\Omega \parallel 10\text{ k}\Omega)} \right) (9\text{ V})$$

$$= \left(\frac{5\text{ k}\Omega}{10\text{ k}\Omega + 5\text{ k}\Omega} \right) (9\text{ V})$$

$$= \left(\frac{5\text{ k}\Omega}{15\text{ k}\Omega} \right) (9)$$

$$= 3\text{ V}$$

Calculate the equivalent output resistance.

$$R_o = (10\text{ k}\Omega) \parallel (10\text{ k}\Omega \parallel 10\text{ k}\Omega)$$

$$= (10\text{ k}\Omega) \parallel \left(\frac{(10\text{ k}\Omega)(10\text{ k}\Omega)}{10\text{ k}\Omega + 10\text{ k}\Omega} \right)$$

$$= (10\text{ k}\Omega) \parallel (5\text{ k}\Omega)$$

$$= \frac{(10\text{ k}\Omega)(5\text{ k}\Omega)}{10\text{ k}\Omega + 5\text{ k}\Omega}$$

$$= 3.333\text{ k}\Omega$$

Therefore, the output resistance, R_o is $3.333\text{ k}\Omega$.

Step 6 of 8

Case (b):

Draw the circuit diagram with series parallel resistors.

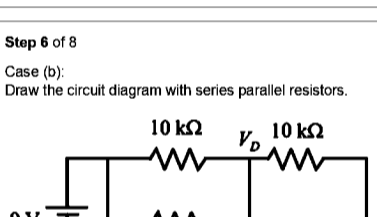


Figure 3

Step 7 of 8

Calculate the voltage, V_D using voltage divider rule.

$$V_D = \left(\frac{10\text{ k}\Omega}{10\text{ k}\Omega + (10\text{ k}\Omega \parallel 10\text{ k}\Omega)} \right) (9\text{ V})$$

$$= \left(\frac{10\text{ k}\Omega}{10\text{ k}\Omega + \left(\frac{10\text{ k}\Omega \times 10\text{ k}\Omega}{10\text{ k}\Omega + 10\text{ k}\Omega} \right)} \right) (9\text{ V})$$

$$= \left(\frac{10\text{ k}\Omega}{10\text{ k}\Omega + 5\text{ k}\Omega} \right) (9\text{ V})$$

$$= \left(\frac{10\text{ k}\Omega}{15\text{ k}\Omega} \right) (9\text{ V})$$

$$= 6\text{ V}$$

Calculate the equivalent output resistance.

$$R_o = (10\text{ k}\Omega \parallel 10\text{ k}\Omega) \parallel (10\text{ k}\Omega)$$

$$= \left(\frac{10\text{ k}\Omega \times 10\text{ k}\Omega}{10\text{ k}\Omega + 10\text{ k}\Omega} \right) \parallel (10\text{ k}\Omega)$$

$$= 5\text{ k}\Omega \parallel 10\text{ k}\Omega$$

$$= \frac{(10\text{ k}\Omega)(5\text{ k}\Omega)}{10\text{ k}\Omega + 5\text{ k}\Omega}$$

$$= 3.333\text{ k}\Omega$$

Therefore, the output resistance, R_o is $3.333\text{ k}\Omega$.

Step 8 of 8

(iii)

Connect two resistors in series as shown in Figure 4.

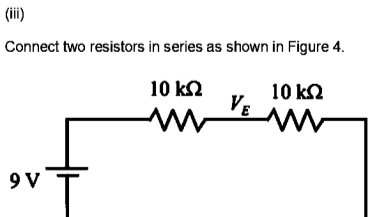


Figure 4

Calculate the voltage, V_E using voltage divider rule.

$$V_E = \left(\frac{10\text{ k}\Omega}{10\text{ k}\Omega + 10\text{ k}\Omega} \right) (9\text{ V})$$

$$= \left(\frac{10\text{ k}\Omega}{20\text{ k}\Omega} \right) (9\text{ V})$$

$$= 4.5\text{ V}$$

Calculate the equivalent output resistance.

$$R_o = (10\text{ k}\Omega \parallel 10\text{ k}\Omega)$$

$$= \frac{(10\text{ k}\Omega)(10\text{ k}\Omega)}{10\text{ k}\Omega + 10\text{ k}\Omega}$$

$$= 5\text{ k}\Omega$$

Therefore, the output resistance, R_o is $5\text{ k}\Omega$.

Therefore, the list of positive sources are 3 V , 4.5 V and 6 V .

For generating 3 V and 6 V , the case (ii) is better than case (i), because it has low

output resistance.